

# Control Systems

G V V Sharma\*

## CONTENTS

### 1 Feedback Circuits

1

**Abstract**—This manual is an introduction to control systems based on GATE problems. Links to sample Python codes are available in the text.

Download python codes using

```
svn co https://github.com/gadepall/school/trunk/
control/codes
```

#### 1 FEEDBACK CIRCUITS

Figure 0 shows a feedback transconductance amplifier implemented using an op amp with open-loop gain  $\mu$ , a very large input resistance, and an output resistance  $r_o$ . The output current  $I_o$  that is delivered to the load resistance  $R_L$  is sensed by the feedback network composed of the three resistances  $R_M$ ,  $R_1$ , and  $R_2$ , and a proportional voltage  $V_f$  is fed back to the negative-input terminal of the op amp. Find  $G$ ,  $H$  and  $T$ . If the loop gain is large, find an approximate expression for  $T$  and state precisely the condition for which this applies. The parameters given are shown in the TABLE.0

Parameter	Value
input resistance	$\infty$
output resistance	$r_o$
Input voltage	$V_s$
Output Voltage	$V_o$

TABLE 0: 1

1. Draw the block diagram and the equivalent circuit for Fig. 0

**Solution:** The equivalent circuit of the amplifier is in Fig. 1

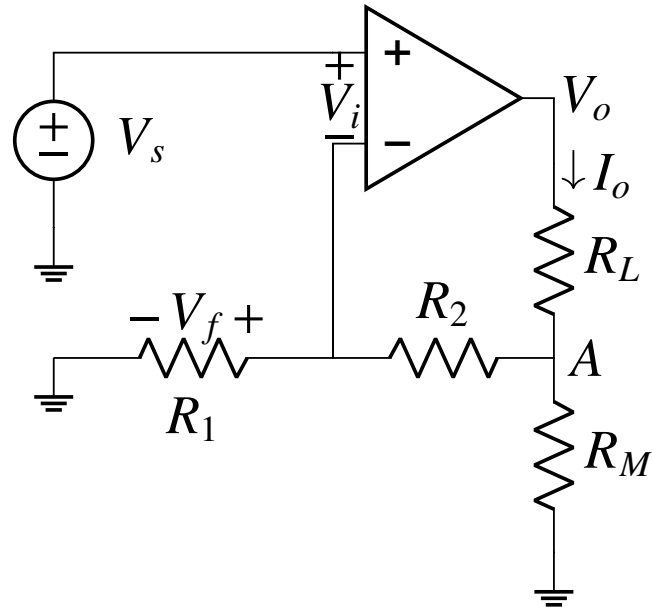


Fig. 0

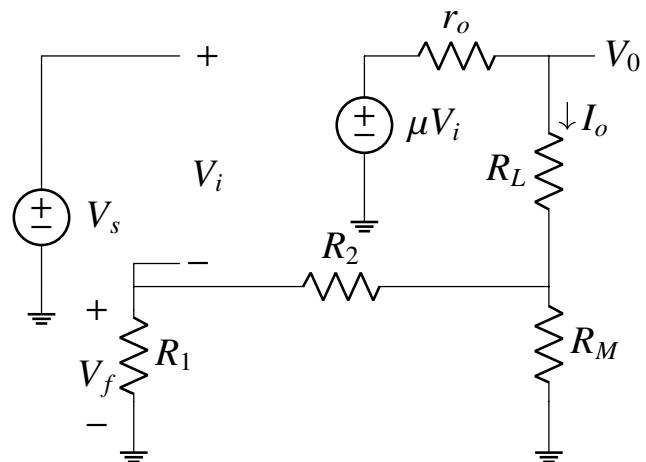


Fig. 1

2. Draw the block diagram and equivalent circuit for  $H$ .

**Solution:** See Fig. 0 and 1.

3. Find  $H$ .

**Solution:** From Fig. 1,

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

$$H = \frac{V_f}{I_o} \quad (3.1)$$

$$= \frac{R_1 R_M}{R_1 + R_2 + R_M} \quad (3.2)$$

4. Find  $G$ .

**Solution:** From Fig. 1,

$$G = \frac{I_o}{V_i} \quad (4.1)$$

$$= \mu \quad (4.2)$$

5. Find  $T$ .

**Solution:**

$$T = \frac{G}{1 + GH} \quad (5.1)$$

$$= \frac{\mu (R_1 + R_2 + R_M)}{R_1 + R_2 + R_M + \mu R_1 R_M} \quad (5.2)$$

$$\approx \frac{1}{H} = \frac{R_1 + R_2 + R_M}{R_1 R_M} \quad (5.3)$$

6. Summarize your results in a table.

**Solution:** See Table 6

Parameters	Definition	For given circuit
Open loop gain	G	$\mu$
Feedback factor	H	$\frac{R_1 R_M}{R_1 + R_2 + R_M}$
Loop gain	GH	$\mu \frac{R_1 R_M}{R_1 + R_2 + R_M}$
Amount of feedback	1+GH	$1 + \frac{\mu R_1 R_M}{R_1 + R_2 + R_M}$
Closed loop gain	T	$\frac{\mu (R_1 + R_2 + R_M)}{R_1 + R_2 + R_M + \mu R_1 R_M}$

TABLE 6

7. Find  $I_o$  for the parameters given in Table 7.

**Solution:** The following code computes the value of  $V_o$  using the fact that

$$I_o = \frac{V_s}{H} \quad (7.1)$$

$$\Rightarrow I_o = \frac{3}{1000} A \quad (7.2)$$

8. Verify your result through spice.

**Solution:** The following readme file provides necessary instructions to simulate the circuit in

Parameter	Value
$R_1$	1000 $\Omega$
$R_2$	1000 $\Omega$
$R_L$	1000 $\Omega$
$R_M$	1000 $\Omega$
$V_s$	1V

TABLE 7

spice.

codes/ee18btech11048/spice/README

The following netlist simulates the given circuit.

codes/spice/feedback.net